

Display control through ESP32 using Arduino Framework

G V V Sharma*

Contents

1	Software	1
2	Setup	1

Abstract—This document shows how to implement a decade counter using the Arduino framework on ESP32.

1 Software

All codes used in this document are available at the following link.

<https://github.com/gadepall/ugv/tree/main/codes/sevenseg>

2 Setup

2.1. Fig.2.1.3 shows all the pins of the ESP32. Connect the pins of the display in Fig. 2.1.1 to the ESP32 using Table 2.1.1. The COM pin should be connected to 3.3V through a resistor.

Display	ESP32
a	32
b	33
c	25
d	26
e	27
f	14
g	12
COM	3.3 V

TABLE 2.1.1: Display-ESP32 connection.

2.2. Now execute the following code using platformio

`codes/sevenseg/src/main.cpp`

*The author is with the Department of Electrical Engineering, IIT Hyderabad, 502285. email:gadepall@ee.iith.ac.in! All content in this manual is released under GNU/GPL.

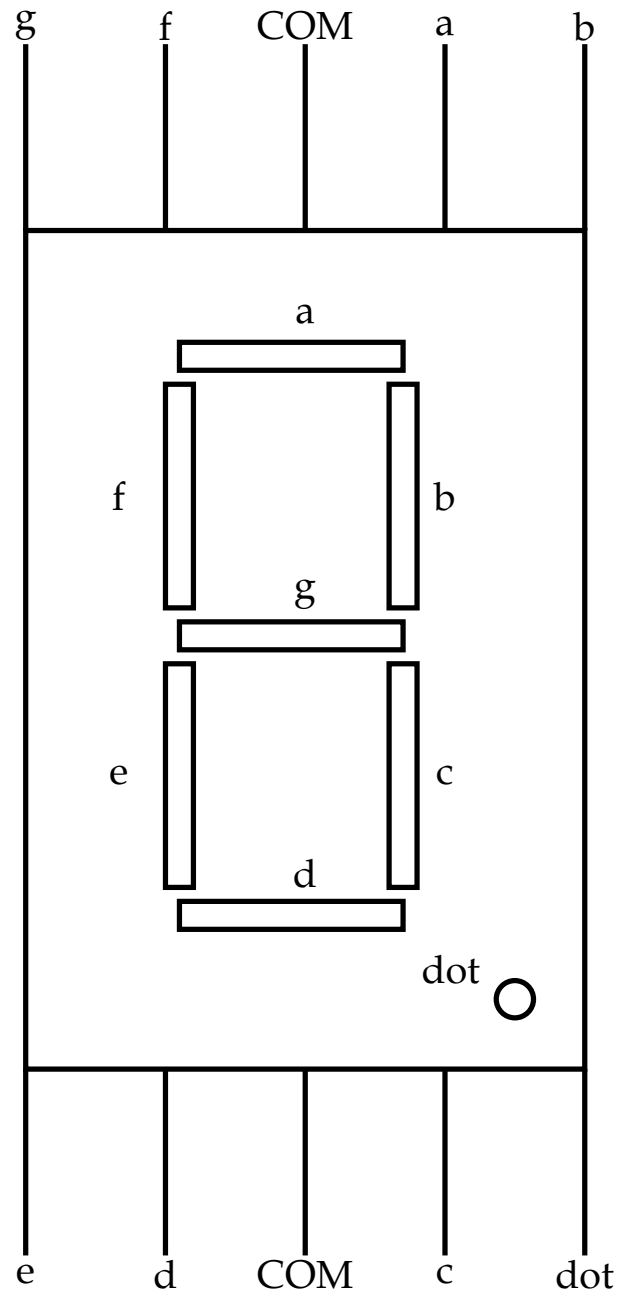


Fig. 2.1.1: Seven Segment Display

Flash firmware.bin obtained upon execution of the above code to the ESP32.

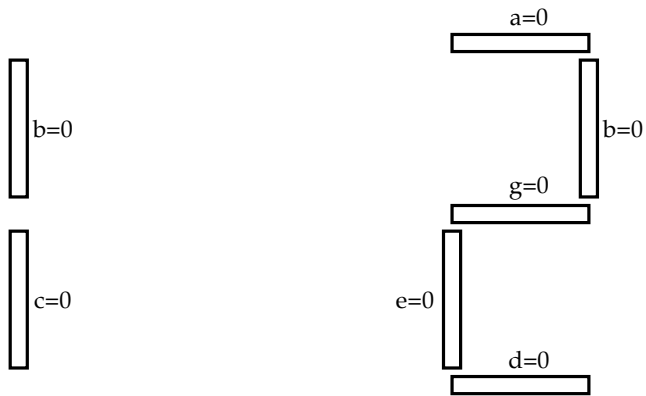


Fig. 2.1.2: Pictorial representation of Table 2.4.1.

2.3. You should see the number 9 on the display. The following function generates this number.

```
sevensseg(0,0,0,0,1,0,0);
void sevensseg(int a,int b,int c
    ,int d,int e,int f,int g)
{
    digitalWrite(32, a);
    digitalWrite(33, b);
    digitalWrite(25, c);
    digitalWrite(26, d);
    digitalWrite(27, e);
    digitalWrite(14, f);
    digitalWrite(12, g);
}
```

2.4. Modify the above program using Table 2.4.1 and Fig. 2.1.2 to display 0-9.

a	b	c	d	e	f	g	decimal
1	0	0	1	1	1	1	1
0	0	1	0	0	1	0	2

TABLE 2.4.1: Decimal number generation on the display.

Fig. 2.1.3: Pin Diagram. Note that the pin diagram may vary depending upon the ESP32 variant.